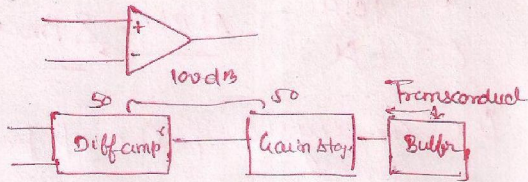


# Single Stage Differential Amplifier Design

Rajeev Kumar Pandey  
Electronics & Communication

## Opm Design

Differential amplifier



## Parameter Requirement


UMC 180nm  
VDD = 1.8  
A ≥ 100 = 40dB  
CL = 10pF

$$GBP \geq 5 \text{ MHz}$$

ICM1 = 1.6V  
ICM2 = 0.8  
SR = 5V/μsec

Power diss < 0.3mW

Diff amp structure

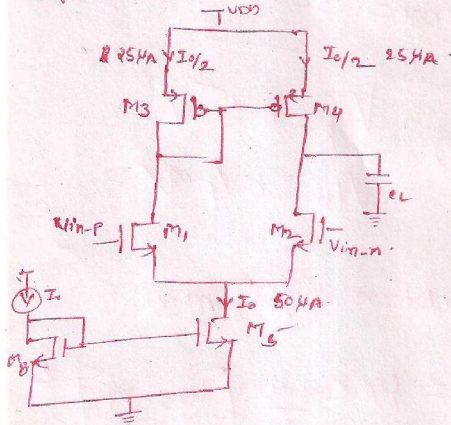

$$M_1 = M_2 \quad M_3 = M_4$$

All the MOSFET are in saturation.


find W/L ratio of all the transistors

1. First find  $I_0$  from S.R. (1)
2.  $M_3$  &  $M_4$  from  $I_{CM1}$
3.  $(W/L)$  of  $M_1$  &  $M_2$  from Gain Bandwidth product
4.  $M_5$   $(W/L)$  from  $I_{CM2}$
5.  $M_5$   $(W/L)$  derived from  $I_0$  &  $M_5$

## Slew rate

maximum rate of change of output voltage  
Slew rate :- rate of change of voltage per unit time.

charging of capacitor from  $M_4$

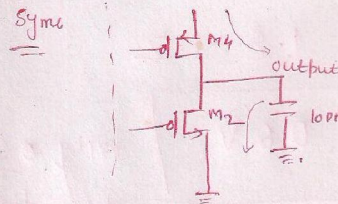

Slew rate happens/measure when one branch is completely off and other is completely on.

$$\frac{dv}{dt} = \frac{I}{C}$$

$$Q = CV$$

$$I = \frac{dQ}{dt} = C \frac{dv}{dt}$$

$$\Rightarrow \frac{dv}{SR} = \frac{I_0}{C_L}$$

$$SR = 5V/\mu\text{sec}$$


$$C_L = 10\text{pF}$$

$$I_0 = \frac{5V \times 10^6 \times 10\text{pF}}{1} = 50\mu\text{A}$$


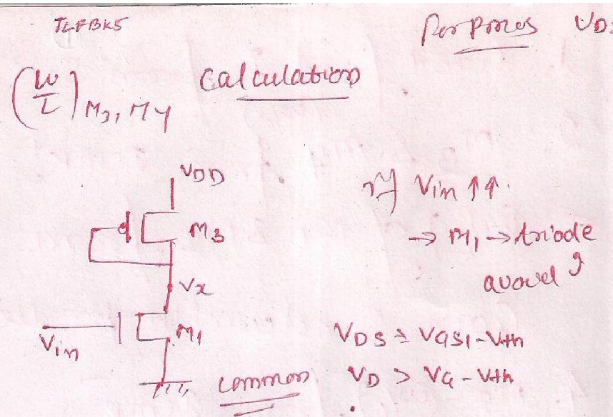
# Single Stage Differential Amplifier Design

Rajeev Kumar Pandey  
Electronics & Communication



maximum input 1.6 (MOSFET not goes to triode)

$V_x > V_{in} - V_{th}$   
 $V_x > 1.6 - 0.45$  (Assume)

$V_x > 1.15 \approx 1.2V$


$V_{DSM3} = V_{DD} - V_x$   
 $V_{DSM3} \approx 1.8 - 1.2$

$V_{DSM3} \approx 0.6V$   
 $= V_{GS3}$

only 0.6V  
drain drop across  $M_3$

$I_{M3} = 25 \mu A$

So find  $Y_{nCOX}$

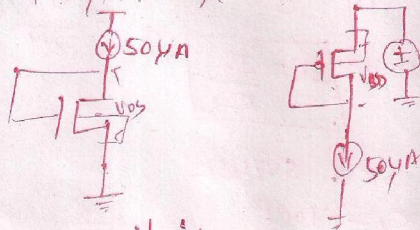

for approx avoid  $\lambda$

$L = 1 \mu m$   
 $L_{in} = 0.18 \mu m$   
 $L = 1 \mu m$

for simulation purpose

$W = 10 \mu m$   
 $L = 1 \mu m$

$1 \mu m \times 8 \mu m$

D.C analysis, D.C op point for PMOS

$\beta_{eff} = 600 \mu$

$Y_{pCOX} = 600 \mu$

$Y_{pCOX} = 60 \mu$

for NMOS

$\beta_{eff} = 2.98 m$  ( $\frac{W}{L} = 10$ )

$Y_{nCOX} \approx 300 \mu$

$V_{th} = 0.5V$   
 $V_{tn} = 0.4V$

Calculation  $(\frac{W}{L})_{M3}$

$I_3 = Y_{pCOX} \frac{W}{2L} [V_{GS} - V_{th}]^2$

$25 \mu = \frac{60 \mu}{2} (\frac{W}{L})_3 [0.6 - 0.5]^2$

$25 \mu = 30 (\frac{W}{L})_3 [0.01]$

$(\frac{W}{L})_3 = 83 \approx 84$  (approx)

$(\frac{W}{L})_3 = (\frac{W}{L})_4 = 84$




# Single Stage Differential Amplifier Design

Rajeev Kumar Pandey  
Electronics & Communication

Calculation of  $m_1$  &  $m_2$


GBP = 5 MHz

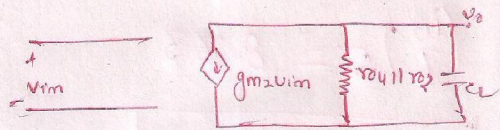

$$\frac{v_o}{r_{o2} || r_{o4}} + \frac{v_o}{s C_L} + g_{m2} v_{in} = 0$$

$$\frac{v_o}{v_{in}} = -\frac{g_m (r_{o2} || r_{o4})}{1 + s C_L (r_{o2} || r_{o4})}$$

Single pole system

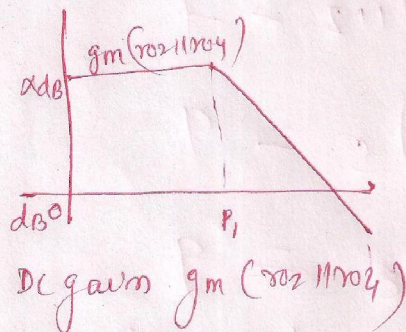

$$P_1 = \frac{1}{(r_{o2} || r_{o4}) C_L}$$

$$GBP = DC \text{ gain} \times P_1$$

$$GBP = \frac{g_m}{s C_L}$$

$$GBP = \frac{g_{m1,2}}{2\pi C_L} \quad (3)$$

$$5 \text{ MHz} = \frac{g_{m1,2}}{2\pi \times 10 \text{ pF}}$$

$$g_{m1,2} = 314.16 \mu\text{A/V}$$

$$I_D = \frac{\mu_n \cos\left(\frac{\omega}{\tau}\right) [v_{gs} - v_t]^2}{2}$$

$$\frac{\partial I}{\partial v_{gs}} = g_m = \mu_n \cos\left(\frac{\omega}{\tau}\right) (v_{gs} - v_t)$$

$$g_m^2 = \left(\mu_n \cos\left(\frac{\omega}{\tau}\right)\right)^2 (v_{gs} - v_t)^2$$

$$g_m^2 = 2 I_D \mu_n \cos\left(\frac{\omega}{\tau}\right)$$

$$\left(\frac{\omega}{\tau}\right)_{1,2} = \frac{g_m^2}{2 I_D \mu_n \cos\left(\frac{\omega}{\tau}\right)}$$

$$\left(\frac{\omega}{\tau}\right)_{1,2} = \frac{(314.16)^2}{2 \times 50 \mu \times 300 \times 10^{-18}}$$

$$\left(\frac{\omega}{\tau}\right)_{1,2} = 6.57$$

$$\left(\frac{\omega}{\tau}\right)_{1,2} = 7$$



# Single Stage Differential Amplifier Design


Rajeev Kumar Pandey  
Electronics & Communication

Summary

$$(W/L)_{3,4}, (W/L)_2 \text{ get$$

$$\frac{K_{nCO}}{2} \left(\frac{W}{L}\right)_5$$

$$I_{cmR^-} = 0.8$$

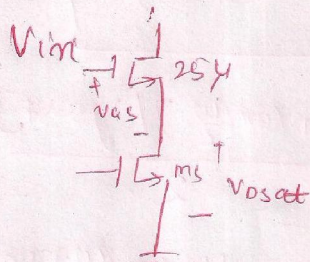

$$V_{dm} > V_{gs1} + V_{dsat}$$

$$0.8 > V_{gs1} + V_{dsat5}$$

$$V_{gs1} = ??$$

$$I_D = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L}\right)_1 [V_{gs1} - V_t]^2$$

$$25\mu = \frac{300\mu \times 7}{2} [V_{gs1} - 0.45]^2$$

$$0.154 = V_{gs1} - 0.45$$

$$V_{gs1} = 0.154 + 0.45$$

$$V_{gs1} = 0.6$$

$$\Rightarrow 0.8 > 0.6 + V_{dsat}$$

$$V_{dsat} \leq 0.2$$

Ids, Vdsat

$$50\mu = \frac{300\mu}{2} \left(\frac{W}{L}\right)_5 (0.2)^2$$

$$\left(\frac{W}{L}\right)_5 = 8.33$$

$$\left(\frac{W}{L}\right)_5 = 9$$

$$\left(\frac{W}{L}\right)_{3,4} = 84$$

$$\left(\frac{W}{L}\right)_{1,2} = 7$$

$$\left(\frac{W}{L}\right)_5 = 9$$

$$\left(\frac{W}{L}\right)_8 = 9$$

Current mirror

40dB difficult to get let do some tracing in simulator



# Single Stage Differential Amplifier Design

Rajeev Kumar Pandey  
Electronics & Communication

